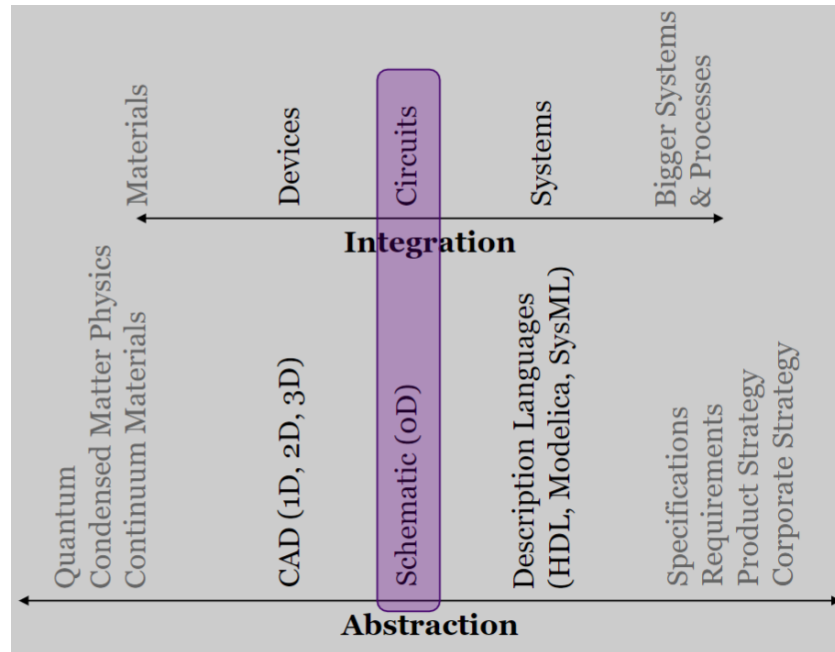


Lecture 1: Intro & Context



C1 Summary

- The International System of Units (SI) enables engineers to communicate in a meaningful way about quantitative results. Table 1.1 summarizes the base SI units; Table 1.2 presents some useful derived SI units. (See pages 30 and 31.)
- Circuit analysis is based on the variables of voltage and current. (See page 33.)
- **Voltage** is the energy per unit charge created by charge separation and has the SI unit of volt ($v = dw/dq$). (See page 34.)
- **Current** is the rate of charge flow and has the SI unit of ampere ($i = dq/dt$). (See page 34.)
- The **ideal basic circuit element** is a two-terminal component that cannot be subdivided; it can be described mathematically in terms of its terminal voltage and current. (See page 34.)
- The **passive sign convention** uses a positive sign in the expression that relates the voltage and current at the terminals of an element when the reference direction for the current through the element is in the direction of the reference voltage drop across the element. (See page 35.)
- **Power** is energy per unit of time and is equal to the product of the terminal voltage and current; it has the SI unit of watt ($p = dw/dt = vi$). (See page 37.)
- The algebraic sign of power is interpreted as follows:
 - If $p > 0$, power is being delivered to the circuit or circuit component.
 - If $p < 0$, power is being extracted from the circuit or circuit component. (See page 38.)

CHAPTER 1: CIRCUIT VARIABLES

- linear circuits have no net power
- **power balances**: total power in circuit == 0

1.1 Electrical Engineering: Overview

- systems that produce/transmit/measure signals
- 5 major classifications
 - **communication** systems: generate/transmit/distribute information
 - **computer** systems: uses electric signals to process information
 - **control** systems: uses electric signals to regulate processes
 - **power** systems: generate & distribute electric power
 - **signal-processing** systems: acts on electric signals that represent information

Circuit Theory

special case of electromagnetic theory; study of static & moving electric charges

1. electrical effects are instantaneous throughout a system (near speed of light)

lumped-parameter system: systems small enough that electrical effects can be assumed simultaneous

- 1/10 of wavelength; $\lambda = \frac{c}{f} = \frac{3 \times 10^8 (m/s)}{\text{frequency}(Hz)}$

2. net charge on every component in system is zero
3. no magnetic coupling between system components

electric circuit: math model that approximates behavior of an actual electric system

1.2 SI Units

Prefix	Symbol	Power
atto	a	10^{-18}
femto	f	10^{-15}
pico	p	10^{-12}
nano	n	10^{-9}
micro	μ	10^{-6}
milli	m	10^{-3}
centi	c	10^{-2}
deci	d	10^{-1}
deka	da	10^1
hecto	h	10^2
kilo	k	10^3
mega	M	10^6
giga	G	10^9
tera	T	10^{12}

Quantity	Basic Unit	Symbol
Length	meter	m
Mass	kilogram	kg
Time	second	s
Electric current	ampere	A
Thermodynamic temperature	degree kelvin	K
Amount of substance	mole	mol
Luminous intensity	candela	cd

Derived Units

Quantity	Unit Name (Symbol)	Formula
Frequency	hertz (Hz)	s^{-1}
Force	newton (N)	$kg \cdot m/s^2$
Energy or work	joule (J)	$N \cdot m$
Power	watt (W)	J/s
Electric charge	coulomb (C)	$A \cdot s$
Electric potential	volt (V)	J/C
Electric resistance	ohm (Ω)	V/A
Electric conductance	siemens (S)	A/V
Electric capacitance	farad (F)	C/V
Magnetic flux	weber (Wb)	$V \cdot s$
Inductance	henry (H)	Wb/A

1.3 Circuit Analysis: Overview

ideal circuit component: mathematical model of an actual electrical component

circuit analysis: uses math techniques to predict behavior of circuit model & its ideal circuit components

physical prototype: actual electric system

1.4 Voltage & Current

Important Characteristics of Electric Charge

- bipolar
- exists in discrete quantities (integer multiples of electronic charge, 1.6×10^{-19})
- attributed to both separation of charge & charges in motion

Voltage: energy per unit charge created by separation

$$V = \frac{dw}{dq} \quad (1.4.1)$$

V: voltage (V), w: energy (J), q: charge (C)

$$1C = 6.242 \times 10^{18} \text{ charges}$$

$$1V = 1 \frac{J}{C}$$

electric current: rate of charge flow

$$I = \frac{dq}{dt} \quad (1.4.2)$$

I: current (A), t: time (s)


$$1A = 1 \frac{C}{s}$$

- made up of discrete moving electrons; considered as one smooth flowing entity (continuous variable)

1.5 Ideal Basic Circuit Element

ideal basic circuit element:

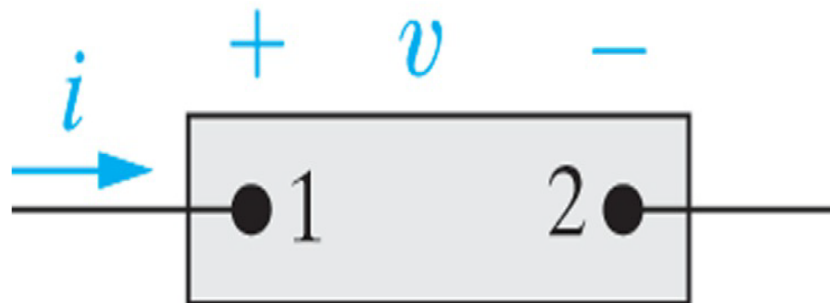1. only two terminals: point of connection to other circuit components
2. described mathematically in terms of current/voltage
3. cannot be subdivided



***passive sign convention:**

Whenever the reference direction for the current in an element is in the direction of the reference voltage drop across the element (as in Fig. 1.5), use a positive sign in any expression that relates the voltage to the current. Otherwise, use a negative sign.

- V @ terminal 1 minus V @ terminal 2
- i: charge from terminal 1 to terminal 2

***I-V characteristics (graph) for any unknown device**


1.6 Power & Energy

net: lines with same voltage


$$P = \frac{dw}{dt} = \left(\frac{dw}{dq}\right)\left(\frac{dq}{dt}\right) = V \times I$$

P: power (W), v: voltage (V), i: current(A)


$$1\text{W} = 1\text{J/s}$$

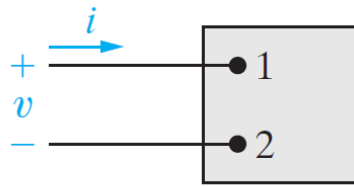


$$(a) \ p = vi$$

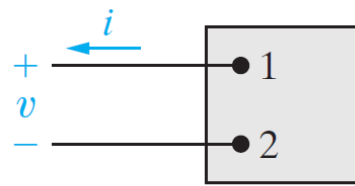

$$(b) \ p = -vi$$

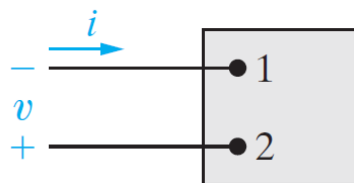

$$(c) \ p = -vi$$

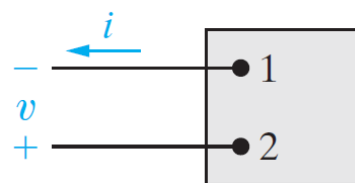

$$(d) \ p = vi$$

Interpreting **algebraic sign of power**: If the power is positive (that is, if $p > 0$), power is being delivered to the circuit inside the box. If the power is negative (that is, if $p < 0$), power is being extracted from the circuit inside the box.